 


1] Explain functioning of JK FlipFlop and SR FlipFlop

JK

Fig -



- It is an Enhancement of SR FF, designed to overcome the indeterminate state problem

- operation mode

i] Hold state
when $J=0, K=0$, previous state

ii] Reset
when $J=0$ & $K=1$

iii] Set
when $J=1$ & $K=0$


iv] Toggle
when $J=1$ & $K=1$

- Application

Counter
Register
Memory
Freq Division

SR

Fig -

 

It is Basic Type of FF that stores single bit of data

operation mode

i] Hold state
when $S=0, R=0$

2] Reset
when $S=0$ & $R=1$

3] Set
when $S=1$ & $R=0$

4] Invalid
when $S=1$ & $R=1$

Basic memory storage

control circuit

Debounce ckt

2] Difference betⁿ FlipFlop and Latches


	FlipFlop	Latch
1]	FlipFlops are bistable device, it has 2 stable States, 0,1	Latch is also Bistable device States Represent as 0,1
2]	o/p changes on Rising edge or falling edge of clock when i/p is changed	o/p changes immediately w/o t input, it monitors i/p continuously
3]	It is edge triggered device	It is level triggered device
4]	It is made up of gates and latches	It is made up of only gates
5]	FlipFlops are slow compared to latches	latches are faster
6]	more power is consumed	less power is consumed
7]	FlipFlops are clocked	Latches can be clocked or clockless
8]	Latches can generate faults or responsive to any fault on enable pin	FlipFlops are protected toward fault
9]	Types JK, SR, D, T FF	JK, SR, D, T latches
10]	It takes more area	It takes less area
11]	FF are synchronous	latches are asynchronous
12]	FlipFlop are more Robust	latches are less Robust than FF
13]	latches are used for Temporal data storage	Flip-Flops are used for permanent data storage

3] Why are latches faster than flipflops


Considering flipflop its internal circuit has more logic level or layers, thus delay are larger in ff that mean delays get added.

- Also latches are transparent during half cycle period & any input changes will reflect immediately on o/p side after combinational delay
- while in case of flipflop it gets updates on rising or falling edges only
It req twice hardware as that of latch to implement

SR Nand latch

 

SR FF


 


4] Explain the use of

i] FlipFlop

ii] Latches

- flipflops and Latches are fundamental building blocks in Digital Electronics.
- They are used for storing and controlling the data
- They serve as memory element for holding data and enabling sequential logic operation
- FF provides Timing control and are used in complex sequential logic application like Counter, Shift Register, state machine
- Latches are simpler and are used for basic data storage & control application
- FlipFlops ability to store and transfer data reliably makes essential components in memory devices, processors

  

S R Nor Latch

5] Why is the Gated SR FF called Asynchronous latch

- Gated SR FF are sometime referred to as asynchronous because they can change their o/p state immediately when their input change
- Gated S-R FF are level-sensitive, meaning their o/p can change as long as the enable signal is active. It is different from edge-triggered FF.
- When the enable signal is active, any changes in the S + R inputs will immediately affect the o/p. This means the o/p responds to the input as soon as they change, not waiting for a clock edge.
- The output can change in direct response to input changes while the enable signal is active, this behavior is considered asynchronous.

Example of Asynchronous Behaviour Gated SR FF


Consider a gated SR FF with enable - E, & i/p S, R

* Enable Active ($E=1$) The FF is open to i/p changes

- i] If $S=1$ & $R=0$, the o/p Q is set to 1
- ii] If $S=0$ & $R=1$, the o/p Q is set to 0
- iii] If $S=0$ & $R=0$, the o/p Q remain in current state
- iv] If $S=1$, $R=1$, the state is usually considered invalid.


Enable Inactive \div The FF ignore i/p changes, & o/p remain unchanged.

6] Implement D-FF using Nand Gate

 

- The edge triggered D FlipFlop has only one i/p terminal
- The D FF may be obtained from S-R FF by inverting or putting inverters between the S and R terminal

 Below Fig shows Logic symbol and Truth table



D	clk	Q	
0	↑	0	Reset
1	↑	1	Set

Ajinkya More

7] Design D-ff using 2:1 Mux



As shown in fig
 master takes input on low phase of clk
 and slave takes input on high phase
 slave always follows the data that master capture

